

## Mark Scheme

Q1.

Question Number	Acceptable answers	Additional guidance	Mark
	D uses $W = \frac{1}{2}CV^2$ so if V is doubled W is 4x	4W	1
	A divides the energy by 4 (rather than multiply) B forgets to square the potential difference and divides C forgets to square the potential difference		

Q2.

Question Number	Answer	Mark
	B	1


Q3.

Question Number	Answer	Mark
	B	1

Q4.

Question Number	Acceptable answers	Additional guidance	Mark
	<ul style="list-style-type: none"> <li>• p.d. across capacitor increases Or p.d. across resistor decreases (1)</li> <li>• p.d. across capacitor increases to 5V (1)</li> <li>• p.d. across resistor starts at 5V and reduces to 0V (1)</li> <li>• Exponentially (1)</li> </ul>		4

Q5.

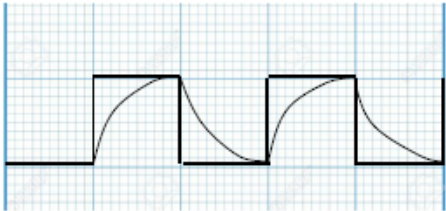Question Number	Acceptable answers	Additional guidance	Mark
	<ul style="list-style-type: none"> <li>• Time axis: one cycle = 50 OR two cycles =100 (1)</li> <li>• Use of time constant = <math>RC</math> (1)</li> <li>• Charging curve, from 25 ms to 50 ms, just about reaching 5V as shown (ecf from their T) (1)</li> <li>• One corresponding discharge curve (1)</li> <li>• Curve should look exponential (1)</li> </ul>	<p><u>Example of calculation</u></p> <p><math>T = 1/f = 1/20 \text{ Hz} = 0.050 \text{ s}</math>            Two cycles = <math>2 \times 0.050 \text{ s} = 0.10 \text{ s} = 100 \text{ ms}</math>            Time Constant = <math>100 \times 50 \times 10^{-6} = 0.005 \text{ s}</math>            In half a cycle (0.025 s) there are <math>0.025 \text{ s} / 0.005 \text{ s} = 5</math> Time constants</p> <p>Ignore anything drawn in the first half cycle</p>  <p>Time period should be marked 50 ms or equivalent</p>	<p>5</p>

Q6.

Question Marks	Acceptable Answers	Additional guidance	Mark
i	<ul style="list-style-type: none"> <li>Use of <math>W = \frac{1}{2} CV^2</math> (1)</li> <li><math>W = 45 \mu\text{J}</math> (1)</li> </ul>	<u>Example of calculation</u> $W = \frac{1}{2} 40\mu\text{F} \times (1.5 \text{ V})^2$ $W = 45 \mu\text{J}$ Alt: Use $Q = CV$ then $E = QV/2$ for MP1	2
ii	<ul style="list-style-type: none"> <li>Use of <math>V = V_0 e^{-t/RC}</math> (1)</li> <li>Time = 0.14 (s) (1)</li> </ul>	<u>Example of calculation</u> $0.5 = e^{-t/5000 \times 40 \times 10^{-6}}$ $\ln 0.5 = -t/0.2$ $t = 0.14\text{s}$	2
iii	<ul style="list-style-type: none"> <li>Use of speed = <math>d/t</math> (1)</li> <li>Speed = <math>3.6 \text{ ms}^{-1}</math> (1)</li> </ul> Allow ecf from ii	Show that value gives $5.0 \text{ ms}^{-1}$ <u>Example of calculation</u> $v = 0.5\text{m}/0.14\text{s}$ $= 3.6 \text{ ms}^{-1}$	2
iv	<ul style="list-style-type: none"> <li>use of <math>s = \frac{at^2}{2}</math> (1)</li> <li><math>s = 9 \text{ cm}</math> (1)</li> </ul> + comment that foil is not broken at its centre (comment consistent with calculation) Allow ecf from ii	Show that value gives 0.049 m <u>Example of calculation</u> $s = \frac{9.81 \text{ ms}^{-2} \times 0.14^2 \text{ s}}{2} = 0.094 \text{ m}$	2

Q7.

Question Number	Answer		Mark
(a)	Use of $Q = CV$ $Q = 0.18 \text{ C}$  <u>Example of calculation</u> $Q = 150 \times 10^{-6} \text{ F} \times 1200 \text{ V}$ $Q = 0.18 \text{ C}$	(1) (1)	2
(b)	Use of $W = \frac{1}{2} CV^2$ Or of $W = \frac{1}{2} QV$ Or of $W = \frac{1}{2} Q^2/C$ $W = 110 \text{ J}$ Allow ecf from (a) if $\frac{1}{2} QV$ or $\frac{1}{2} Q^2/C$ used  <u>Example of calculation</u> $W = \frac{1}{2} \times 150 \times 10^{-6} \text{ F} \times (1200 \text{ V})^2$ $W = 108 \text{ J}$	(1) (1)	2
(c)(i)	$R = 86 \text{ } (\Omega)$  <u>Example of calculation</u> $R = V/I = 1200 \text{ V} / 14 \text{ A}$ $R = 85.7 \text{ } \Omega$	(1)	1
(c)(ii)	$Q = 0.25 Q_0$ Or $Q = 0.045 \text{ C}$ Use of $RC$ (0.013 s) Use of $Q = Q_0 e^{-t/RC}$ to give $t = 0.018 \text{ s}$ (show that value will give $t = 0.019 \text{ s}$ )  [ Use of $\ln 4$ gives the correct answer if the $-$ sign is ignored , scores 1 for use of $RC$ use of $\frac{3}{4}Q \rightarrow 3.7 \times 10^{-3} \text{ s}$ scores 1 mark]  <b>Or</b> Use of $RC$ Use of $2 \times 0.69 \times RC$ $t = 0.018 \text{ s}$  <u>Example of calculation</u> $Q = 0.25 Q_0$ $Q = Q_0 e^{-t/RC}$ $0.25 Q_0 = Q_0 e^{-t/RC}$ $\ln(0.25) = -t / (86 \text{ } \Omega \times 150 \times 10^{-6} \text{ F})$ $t = 0.0178 \text{ s}$	(1) (1) (1)	3
(c)(iii)	Same charge (flows for shorter time) <b>OR</b> (Same charge flows for) shorter time	(1)	1

Q8.



Question Number	Answer	Mark
(a)(i)	Capacitor, resistor, supply and switch all in series (ignore voltmeter) Voltmeter directly across capacitor	(1) (1) 2
(a)(ii)	Datalogger allows large number of readings to be taken Or graph can be plotted directly/automatically Or simultaneous reading of $t$ and $V$ can be taken Or idea that people can't record quickly enough, (treat as neutral accuracy, precision misreading or human reaction time)	(1) 1
(b)	Use of $C = Q/V$ $Q = 5.0 \times 10^{-4} \text{ C}$  <u>Example of calculation</u> $Q = 100 \times 10^{-6} \text{ F} \times 5.0 \text{ V}$ $Q = 5.0 \times 10^{-4} \text{ C}$	(1) (1) 2
(c)(i)	Use of $I = \Delta Q / \Delta t$ e.c.f their value of $C$ from (b) $I = 0.05 \text{ A}$ (accept recalculation of $Q$ using $V = 4.90$ or $4.95 \text{ V}$ )  <u>Example of calculation</u> $I = 5.0 \times 10^{-4} \text{ C} / 10 \times 10^{-3} \text{ s}$ $I = 0.05 \text{ A}$	(1) (1) 2
(c)(ii)	tangent drawn at $t = 0$ $\Delta V / \Delta t = 2000 - 3300 \text{ V s}^{-1}$ Initial current = $0.22 - 0.28 \text{ A}$ (MP2 & 3 can be scored even if no tangent drawn) (No credit for exponential calculation)  <u>Example of calculation</u> $\Delta V / \Delta t = 1.1 \text{ V} / 0.5 \text{ ms} = 2200 \text{ V s}^{-1}$ $I = (\Delta V / \Delta t) \times C$ $I = 2200 \text{ V s}^{-1} \times 100 \times 10^{-6} \text{ F}$ $I = 0.22 \text{ A}$	(1) (1) (1) 3
(c)(iii)	Use of $V = IR$ using answer from (ii) correct evaluation of $R$ ( $5\text{V}$ used with current range in (ii) gives $18 - 23 \Omega$ )  <u>Example of calculation</u> $5 \text{ V} = 0.22 \text{ A} \times R$ $R = 23 \Omega$	(1) (1) 2
<b>Total for question</b>		<b>12</b>

Question Number	Answer	Mark
(a)	Use of $C=Q/V$ (1) $V=15\text{ V}$ (1) Use of $W=QV/2$ Or $W=CV^2/2$ Or $W=Q^2/2C$ (1) $W=2.5 \times 10^{-5}\text{ J}$ (1) (candidates who use $6.6 \times 10^{-6}\text{ C}$ can only score MP1 and MP3)  <u>Example of calculation</u> $V=Q/C=3.3 \times 10^{-6}\text{ C} / 220 \times 10^{-9}\text{ F}$ $V=15\text{ V}$ $W=QV/2=(3.3 \times 10^{-6}\text{ C} \times 15\text{ V})/2$ $W=2.5 \times 10^{-5}\text{ J}$	4
(b)	$Q=0.2 Q_0$ Or $Q=6.6 \times 10^{-7}\text{ C}$ (1) Use of $Q=Q_0 e^{-t/RC}$ (1) $t=7.1\text{ s}$ (1) (candidates who use $Q=0.8 Q_0$ can only score MP2)  <u>Example of calculation</u> $Q=0.2 Q_0$ $Q=Q_0 e^{-t/RC}$ $0.2 Q_0=Q_0 e^{-t/RC}$ $\ln(0.2)=-t/(20 \times 10^6 \Omega \times 220 \times 10^{-9}\text{ F})$ $t=7.1\text{ s}$	3

(c)	<b>Either</b> refers to $W=Q^2/2C$ Or $W \propto Q^2$ (1) If $Q$ halves, $W \rightarrow Q^2/8C$ Or halving $Q$ quarters $W$ (1) (Since $W$ becomes a quarter in the time for $Q$ to half) it takes less time for the energy to halve than the charge to halve. (dependent mark on either MP1 or MP2) (1)  <b>Or</b> Refers to $W=QV/2$ (1) $Q$ and $V$ both decrease over time (1) $W$ will decrease faster so takes less time to half in value. (dependent mark on either MP1 or MP2) (1)	3
(d)	Synchronous readings Or data logger records readings at exact time (1) Or voltmeter and stop watch need 2 people and data logger only one  More readings can be taken in a shorter time Or higher sampling rate (1)	2
<b>Total for question</b>		<b>12</b>

Q11.

Question Number	Answer	Mark
(a)	The capacitor stores charge Or capacitor charges from the supply The idea that the capacitor doesn't fully discharge before being recharged.	(1) (1) 2
(b)(i)	$(6.4 + 4.4)/2 = 5.4 \text{ V}$	(1) 1
(b)(ii)	Use of $V = IR$ Average $I = 5.4 \text{ V}/(2.2 \times 10^3 \Omega) = 2.5 \times 10^{-3} \text{ A}$ ecf value from (b)(i)	(1) (1) 2
(b)(iii)	Time = 17 ms or 17.5 ms	(1) 1
(b)(iv)	Use of $Q = It$ Use of $C = Q/V$ Use of $\Delta V = 2.0 \text{ V}$ $C = 21 \mu\text{F}$ (ecf values of $I$ and $t$ from above)  <u>Example of calculation</u> $Q = 2.5 \times 10^{-3} \text{ A} \times 17 \times 10^{-3} \text{ s} = 4.25 \times 10^{-5} \text{ C}$ $C = 4.25 \times 10^{-5} \text{ C} / 2.0 \text{ V}$ $C = 21 \mu\text{F}$	(1) (1) (1) (1) 4
(c)	Uses a larger capacitance  Because a larger time constant is needed Or stores more charge Or less $\Delta V \rightarrow \Delta Q/C$	(1)   (1) 2
<b>Total for question</b>		<b>12</b>

Q12.

Question Number	Answer	Mark
(a)(i)	Use of $Q = CV$ $Q = 3900 \text{ (C)}$  <u>Example of answer</u> $Q = 1500 \text{ F} \times 2.6 \text{ V}$ $Q = 3900 \text{ C}$	(1) (1)  2
(a)(ii)	Straight line through the origin Passing through 2.6 V and answer to (a)(i) or 4000 C	(1) (1)  2
(a)(iii)	Use of $W = QV/2$ Or $W = CV^2/2$ Or use of area under graph $W = 5.1 \text{ kJ}$ (use of 4000 C gives $W = 5.2 \text{ kJ}$ (allow ecf from (a)(i))  <u>Example of answer</u> $W = 3900 \text{ C} \times 2.6 \text{ V} / 2$ $W = 5070 \text{ J}$	(1) (1)  2
(b)(i)	Exponential decay Current decreases by equal fractions in equal time intervals	(1) (1)  2
(b)(ii)	See attempt of $I_0/e$ Finds time (accept 0.75-0.80s) Use of $\tau = RC$ $R = 0.0005 \Omega$ <b>Or</b> Finds the time for $I_0$ to half Uses $t_{1/2} = \tau \ln 2$ Use of $\tau = RC$ $R = 0.00050 - 0.00053 \Omega$ <b>Or</b>	(1) (1) (1) (1)  (1) (1) (1) (1)  (1) (1) (1) (1)
	See attempt of 37% of 5400 A Finds time (accept 0.75 to 0.80 s) Use of $\tau = RC$ $R = 0.0005 - 0.00053\Omega$ <b>Or</b> Draws tangent at $t = 0$ to meet time axis. Records intercept of tangent with axis (accept 0.6 s - 0.9 s) Use of $\tau = RC$ $R = 0.0004 \Omega - 0.0006 \Omega$ <b>Or</b> reads a value off the y-axis and corresponding time Subs into formula using 5400 (A) to find RC Substitutes for C to find R $R = 0.00050 \Omega - 0.00058 \Omega$  <u>Example of calculation</u> 37% of 5400 A is 1998 A Time to fall to this value is 0.75 s $RC = 0.75 \text{ s}$ $R = 0.75 \text{ s} / 1500 \text{ F} = 0.0005 \Omega$	(1) (1) (1) (1)  (1) (1) (1) (1)  (1) (1) (1) (1)  (1) (1) (1) (1)
		4

(c)	<p><b>Max 3</b></p> <p>Ultracapacitor used for: overtaking <b>Or</b> going up a hill <b>Or</b> starting (from rest) <b>Or</b> accelerating. (1) Because this requires a large <u>current/power</u>. (1) Batteries used for travelling at constant speed (1) Because this requires a small <u>current/power</u> for a longer time (1)</p>	<b>3</b>
<b>Total for question</b>		<b>15</b>